

MIT Splash 2021

Transistors!

Class Notes

(taught by Matthew Cox & Julian Espada)

our email address:

E14835 - teachers@esp.mit.edu

Voltage
"push" on electrons





Current

$5A = \frac{5C}{s}$



~~1C = 1.6 * 10¹⁹~~

A diagram showing a horizontal arrow pointing to the right, representing current flow. Above the arrow is a small circle with a dot inside, representing a positive charge carrier.


V-I Relations

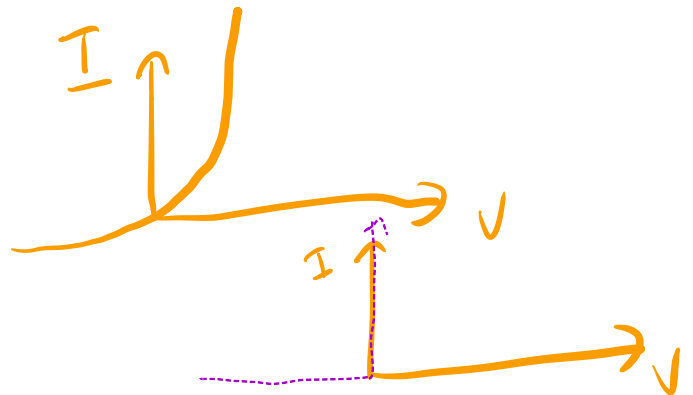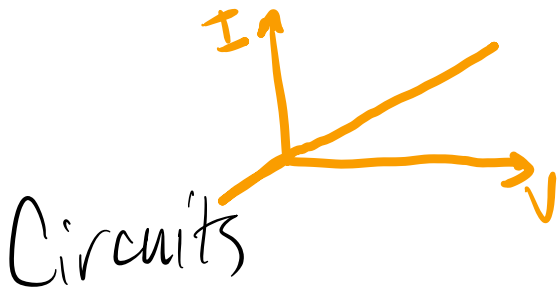

Circuits

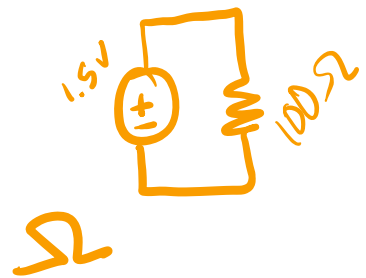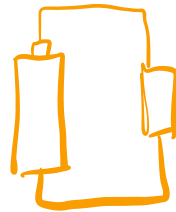

Schematics

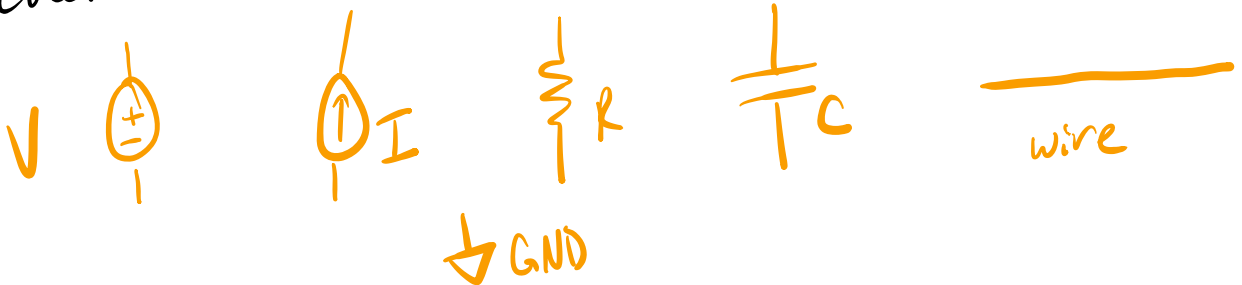

- Two common types of transistors: MOSFETS and BJT's. We'll only consider BJT's in this class.

- Physics of how transistors work is key and the scope of this class. Email us after if you want to learn about transistor physics!

BJT's (bipolar junction transistors)

Two types: NPN and PNP. Type determined by chemical composition.

NPN



Schematic symbol:

PNP

Schematic symbol:

(b = base, c = collector, e = emitter)



Important values: V_{BE} , V_{CE} , I_c

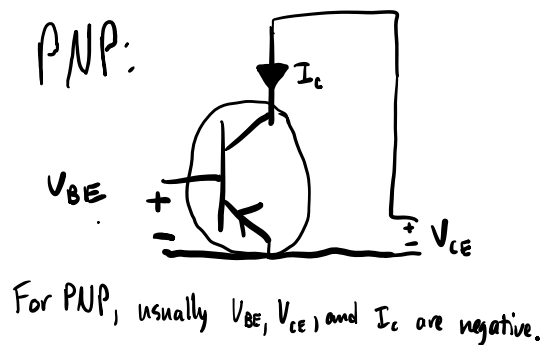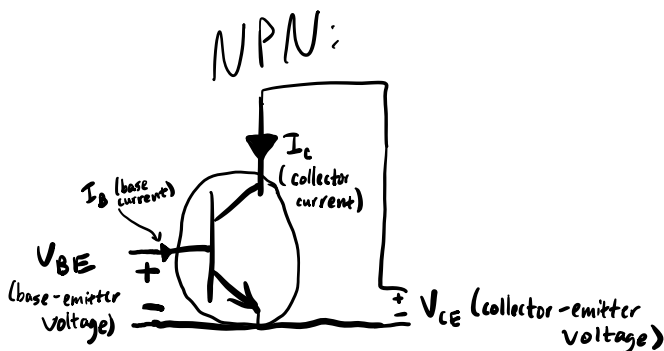


For PNP, usually V_{BE} , V_{CE} and I_c are negative.

Modes of operation (plots of I_c vs V_{CE})

NPN:

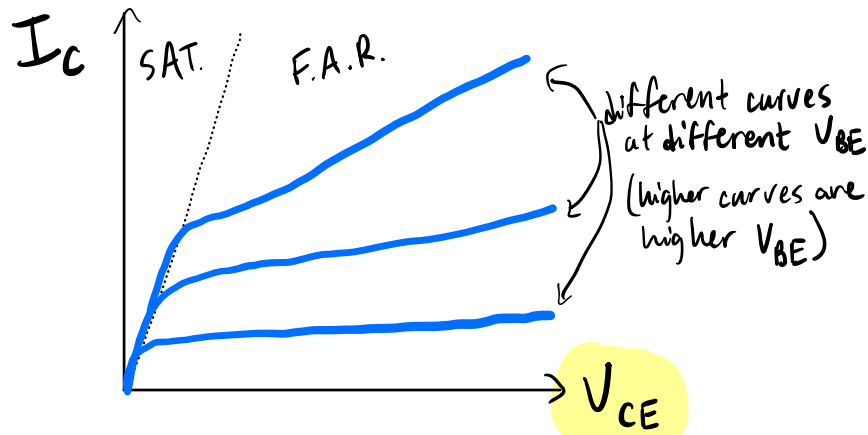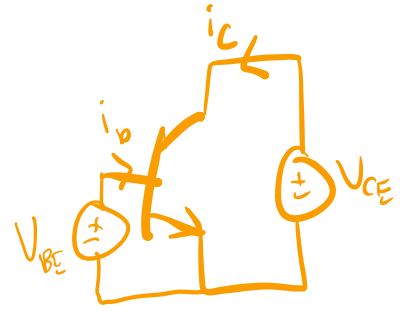

PNP:

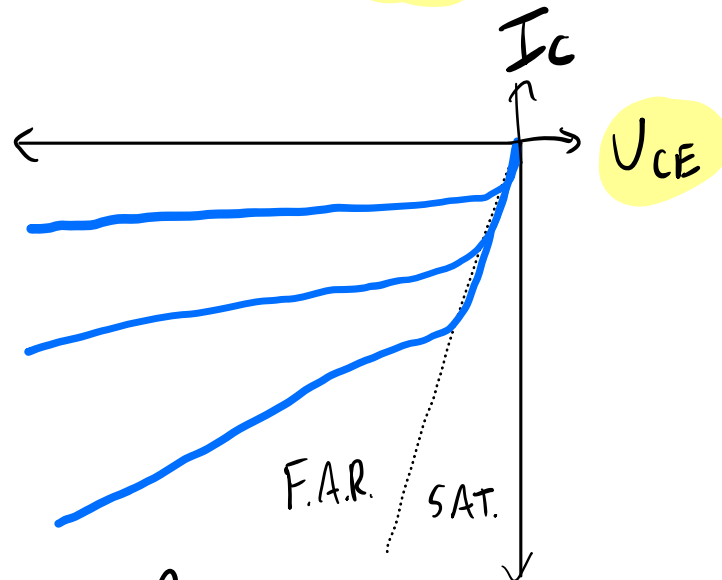


SAT: Saturation Region

F.A.R.: Forward Active Region


We'll only consider F.A.R. in this class.

I_C vs. V_{CE} measured on actual transistors:

NPN:

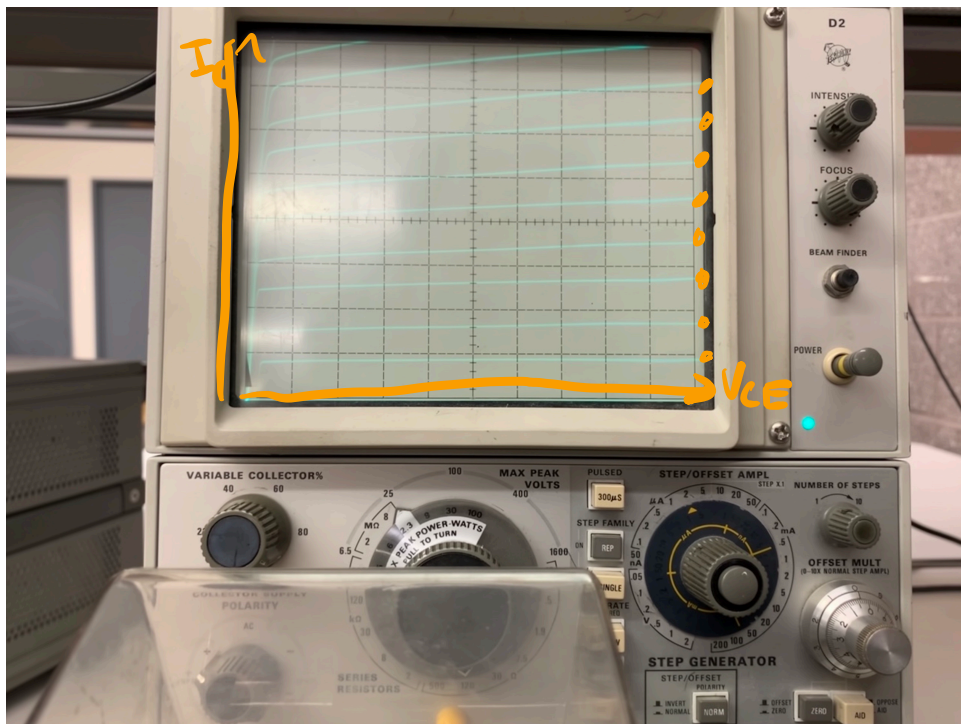

PNP:

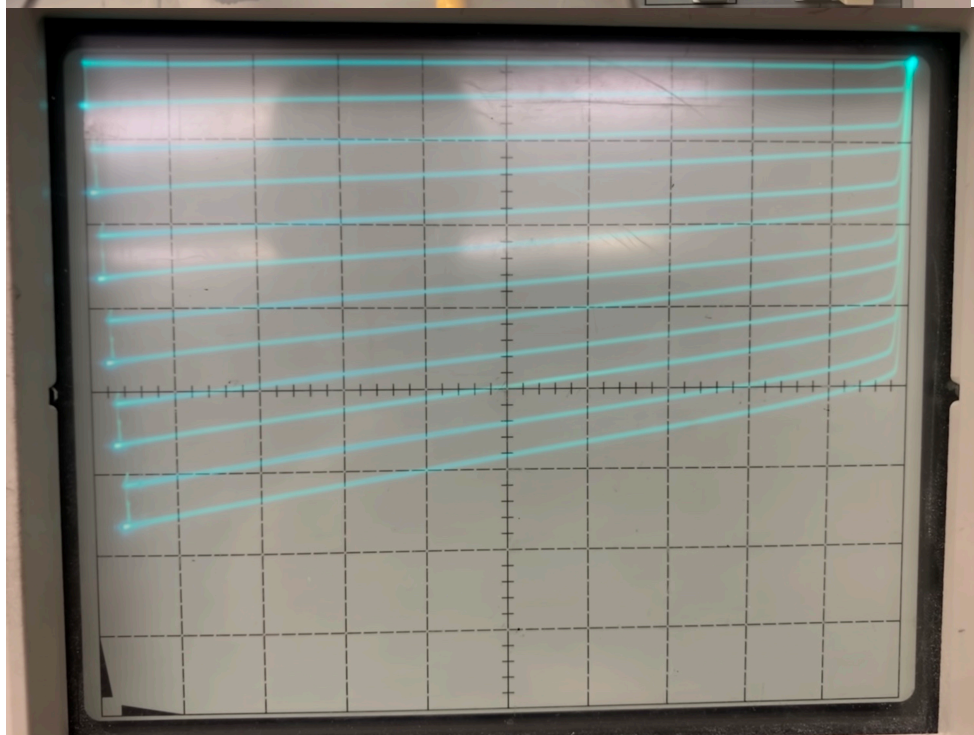

(I took these measurements on a Tektronix 577 curve tracer in Nov. 2019)

In F.A.R.:

(NPN)

$$I_c = I_s e^{\frac{V_{BE}}{V_{th}}} \left(1 + \frac{V_{CE}}{V_A} \right)$$



Annotations:

- I_c : Collector current
- I_s : "Saturation current" (based on device dimensions and chemistry; typically near $1 \mu A$ ($10^{-6} A$)).
- e : Euler's constant (2.718...)
- V_{BE} : Base-Emitter voltage
- V_{th} : "thermal voltage" $V_{th} = \frac{k_B T}{q}$ (Boltzmann's constant k_B , Temperature T , charge of electron q). At room temp, $V_{th} \approx 25 mV$.
- V_A : "Early voltage" (named after James Early). Often, $V_{CE} \ll V_A$ (so $1 + \frac{V_{CE}}{V_A} \approx 1$) so we sometimes can ignore this term.

And $I_c = \beta_0 I_b$ for some constant β_0 ("current gain").
 (Often, β is in the range 10 to 1000. We sometimes assume $I_b = 0$, since I_b is sometimes too small to affect the circuit if β is very high.)

For PNP, $I_c = I_s e^{-\frac{V_{BE}}{V_{th}}} \left(1 + \frac{V_{CE}}{V_A} \right)$ (and I_s and V_A are negative).

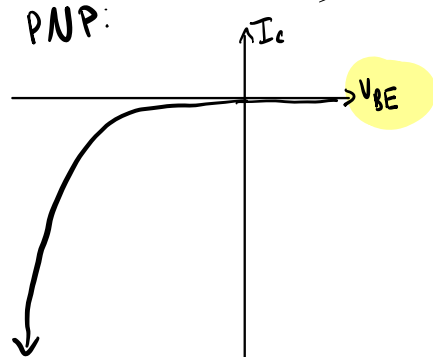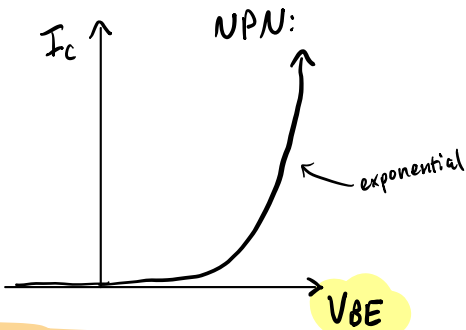
Plots (at constant V_{CE} ; V_{CE} is high enough that BJTs are in F.A.R.)



In this class, we'll consider NPN only
 (but PNP operates the same way, just with some negative signs)

Small-Signal Parameters

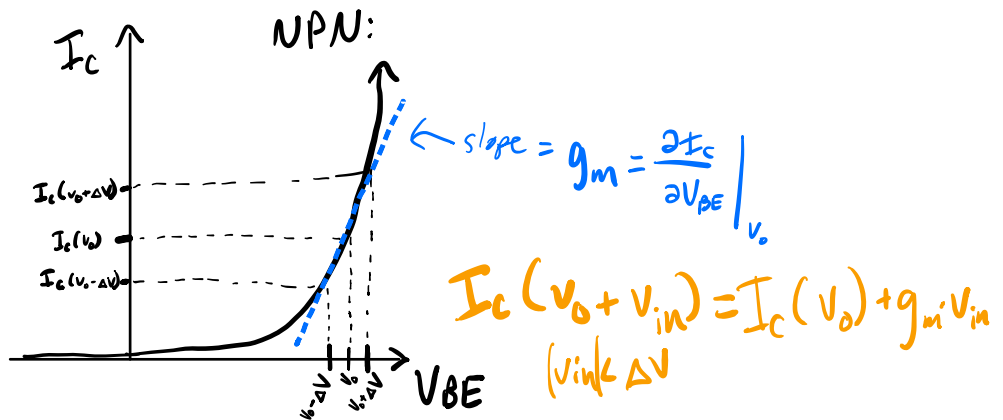What if we keep V_{BE} close to some constant value?



Then the I_C vs. V_{BE} curve is nearly linear!

We say its slope is g_m (transconductance).

$$g_m = \left. \frac{\partial I_C}{\partial V_{BE}} \right|_{V_0} = \frac{\partial}{\partial V_{BE}} I_S e^{\frac{V_{BE}}{V_{th}}} \Big|_{V_0} \quad (\text{ignore Early effect})$$

($= \frac{1}{r}$)

$$= \frac{I_S}{V_{th}} e^{V_0/V_{th}} = \frac{I_C(V_0)}{V_{th}}$$


@ 1mA
 $g_m = \frac{1}{25 \Omega}$
 (where $I_C(V_0)$ is the current I_C when $V_{BE} = V_0$, it's not $I_C \times V_0$).

This linear behavior makes analysis easier!



We call the set of parameters around which we linearize (like V_0 , I_C , etc.) the operating point.

But how to make V_{BE} stay in a small range around some V_0 so we can analyze linearly? And how to set this V_0 ?
 we call techniques for this biasing.


One way: voltage source

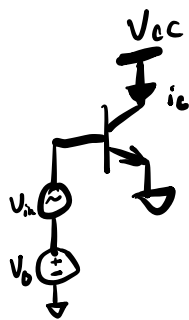

$$V_{BE} = V_{in} + V_0$$

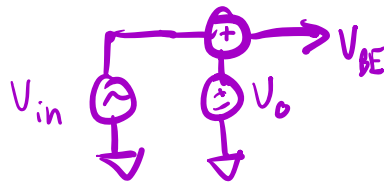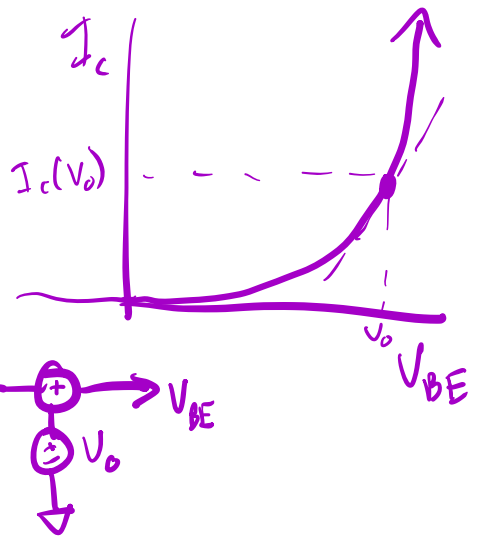

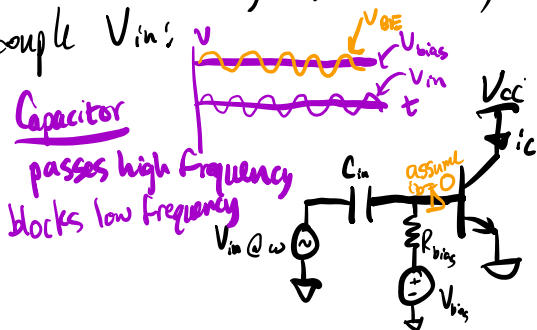But it's hard to implement a voltage source with a floating reference, so we can capacitatively couple V_{in} :



Capacitor
 passes high frequency
 blocks low frequency

Exercise for reader: why do we need R_{bias} ? why can't we directly connect V_{bias} to the base? Think about it now; we'll answer it soon.

Capacitive coupling only works for AC input signals, so it's not uniformly applicable. But it's a simple solution, so it's often used.

Let's compute V_{BE} in the capacitatively coupled case:

Assume $I_b = 0$.

$$V_{BE} = V_{bias} + V_{in} \left(\frac{R_{bias}}{R_{bias} + jX_{C_{in}}} \right) = V_{bias} + V_{in} \left(\frac{R_{bias}}{R_{bias} + \frac{1}{j\omega C_{in}}} \right)$$

Then if $R_{bias} \gg \frac{1}{\omega C_{in}}$ (i.e. frequency is sufficiently high), $V_{BE} \approx V_{bias} + V_{in}$, as desired.


How to generate V_{bias} ?

Typically with a voltage divider from V_{CC} to ground:



Thevenin eq.
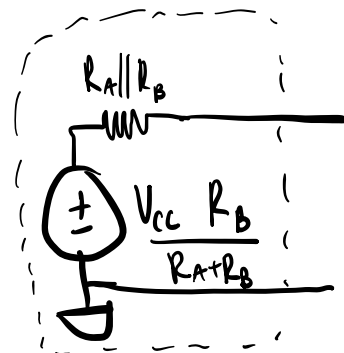
$$R_{th} = R_A \parallel R_B = \frac{1}{\frac{1}{R_A} + \frac{1}{R_B}}$$



A voltage source with resistor, like we want!



Potential further topics (based on interest and time):

- emitter degeneration
- single - BJT amplifiers
 - Common emitter, common base, Emitter follower
- input and output resistance
- differential pairs
- parasitics and frequency response
- Common two-transistor amplifiers, and when to use them
 - Emitter follower \rightarrow common emitter
 - Cascode
- current mirrors
- actively loaded amplifiers
- and much more!

Single-BJT Amplifiers

3 variants

- Common-Emitter

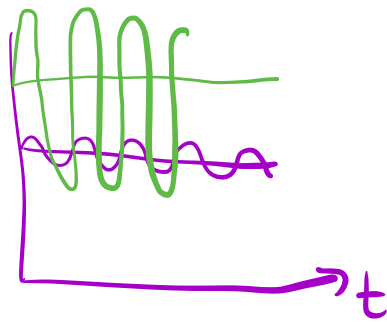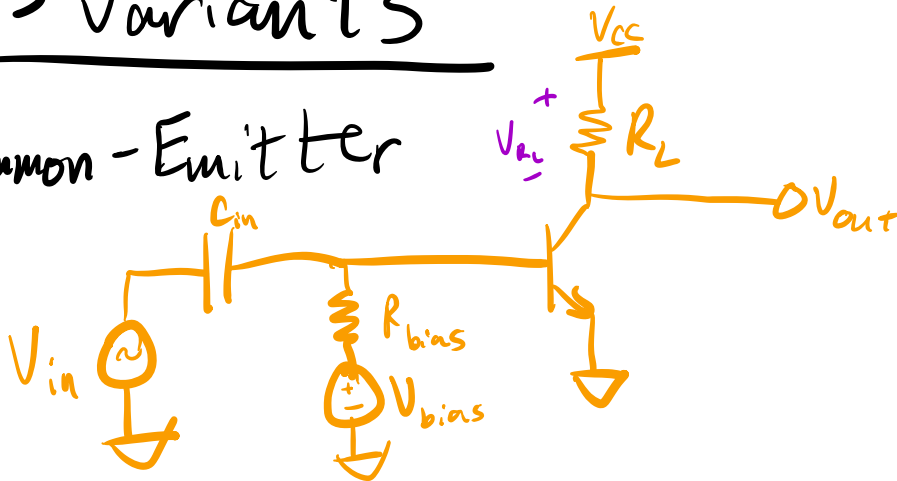

$$I_c = g_m V_{in}$$


$$V_{R_L} = I_{R_L} R_L$$

$$V_{R_L} = g_m V_{in} R_L$$

$$V_{out} = V_{cc} - V_{R_L}$$

$$\begin{aligned} &= V_{cc} - g_m V_{in} R_L \\ \frac{dV_{out}}{dV_{in}} &= -g_m R_L \end{aligned}$$

- Emitter Follower (common collector)

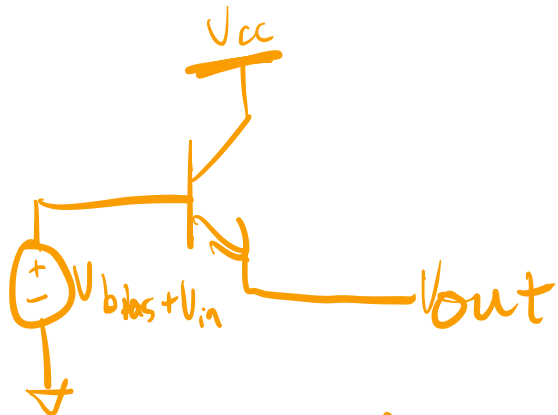

Voltage buffer


$$a_v = 1$$

assume I_C is mostly fixed

→ $V_{BE} \approx \text{constant}$

$$\rightarrow V_{out} = V_{bias} + V_{in} - V_{BE} \quad \left(\frac{\partial V_{out}}{\partial V_{in}} \approx 1 \right)$$

- Common-Base

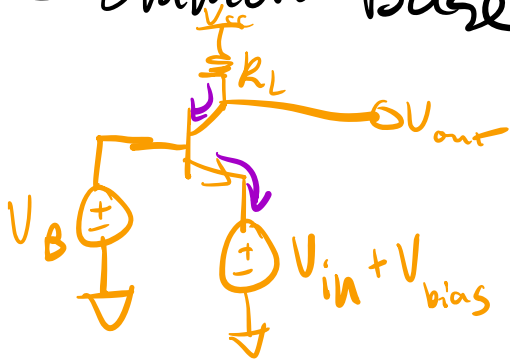

current buffer